

HALL TICKET NUMBER

--	--	--	--	--	--	--	--	--	--

PACE INSTITUTE OF TECHNOLOGY & SCIENCES::ONGOLE  
(AUTONOMOUS)

II B.TECH I SEMESTER END REGULAR/SUPPLEMENTARY EXAMINATIONS, JAN - 2023  
ELECTRICAL CIRCUIT ANALYSIS  
(EEE Branch)

Time: 3 hours

Max. Marks: 60

Note: Question Paper consists of Two parts (Part-A and Part-B)

PART-A




Answer all the questions in Part-A (5X2=10M)




Q.No.	Questions	Marks	CO	KL
1	a) State Thevenin's theorem.	[2M]	1	1
	b) At a particular instant, the R phase voltage of a balanced three phase system is 40V, and Y phase voltage is - 80 V. What will be the voltage of B phase at that instant?	[2M]	2	1
	c) Write the properties of series resonance	[2M]	3	1
	d) What is reciprocal condition of ABCD Parameters?	[2M]	4	1
	e) How do you form tree and co-tree in the network topology?	[2M]	5	1

PART-B

Answer One Question from each UNIT (5X10=50M)

Q.No.	Questions	Marks	CO	KL
UNIT-I				
2.	Using mesh analysis, find the current flow through the 50V source in the network of figure -1	[10M]	1	3
<p style="text-align: center;">Figure -1</p>				
OR				
3.	State compensation theorem. In the network shown in below figure-2, the 2 ohm resistor is changed to 8 ohm. Determine the resulting change in current through the (3+j4) ohm impedance branch using compensation theorem.	[10M]	1	1
<p style="text-align: center;">Figure -2</p>				

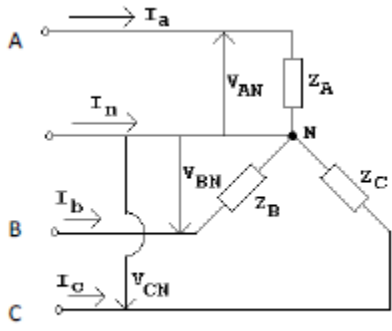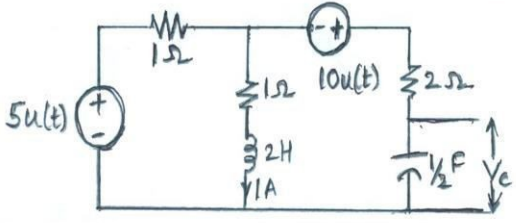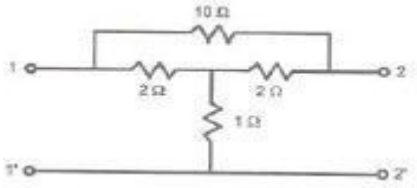UNIT-II					
4.	a)	Draw phasor diagram of currents for a balanced delta-connected supply system and Establish relation between line currents and phase currents	[5M]	2	2
	b)	A balanced 3- phase, 3-wire 50 Hz, 220 V supply is given to a load consisting of three impedances each of $(3+j4)$ ohms connected in star. Determine the line and phase voltages and also currents.	[5M]	2	2
OR					
5.		The unbalanced star connected load shown in Figure -3 has balanced voltages of 100 V with abc sequence. Calculate the line currents and neutral currents. Take $Z_A = 15$ Ohm, $Z_B = (10 + j5)$ Ohm, $Z_C = (6-j8)$ Ohm.	[10M]	2	3
					
		Figure – 3			
UNIT-III					
6.	a)	What is Coefficient of Coupling and derive an expression for the Coefficient of Coupling 'k'	[5M]	3	2
	b)	Compare series resonance with parallel resonance.	[5M]	3	2
OR					
7.		Find the voltage across the capacitor shown in Figure -4 using Laplace transform. Verify with time domain analysis.	[10M]	3	3
					
		Figure -4			
UNIT-IV					
8.		Obtain the Z- parameters and ABCD parameters of the circuit shown in Figure – 5 .	[10M]	4	3
					
		Figure – 5			
OR					

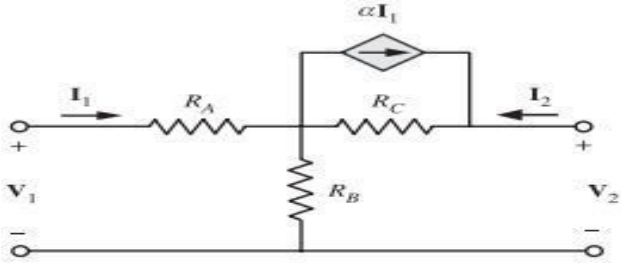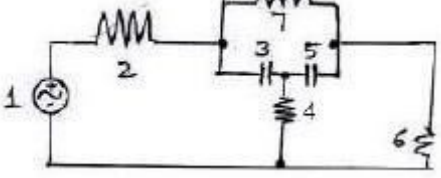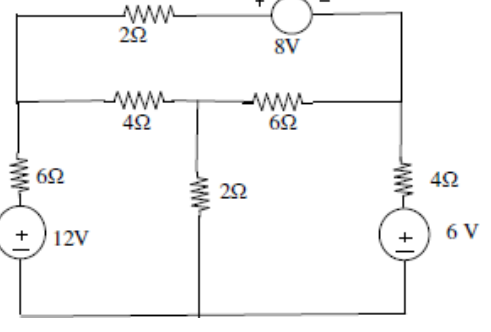9.		<p>For the network shown in Figure – 6 below find hybrid parameters (the dependent source is of <math>\alpha I_1</math>)</p>  <p style="text-align: center;">Figure – 6</p>	[10M]	4	3
UNIT-V					
10.	a)	Define the Basic cut set and tie set matrices for planar networks	[5M]	5	2
	b)	<p>Draw the graph of the network shown in Figure – 7 and write down the tie-set Matrix</p>  <p style="text-align: center;">Figure – 7</p>	[5M]	5	2
OR					
11.		<p>Find out currents through and voltages across all branches of the network shown in figure - 8, with the help of tie-set schedule.</p>  <p style="text-align: center;">Figure – 8</p>	[10M]	5	3

\*\*\*\*\*

