

Code No: P21EET01

HALL TICKET NUMBER

--	--	--	--	--	--	--	--	--	--





PACE INSTITUTE OF TECHNOLOGY & SCIENCES::ONGOLE  
(AUTONOMOUS)

II B.TECH I SEMESTER END REGULAR EXAMINATIONS, JAN - 2023  
ELECTRICAL CIRCUIT ANALYSIS-II  
(EEE BRANCH)

Time: 3 hours

Max. Marks: 70

Answer all the questions from each UNIT (5X14=70M)

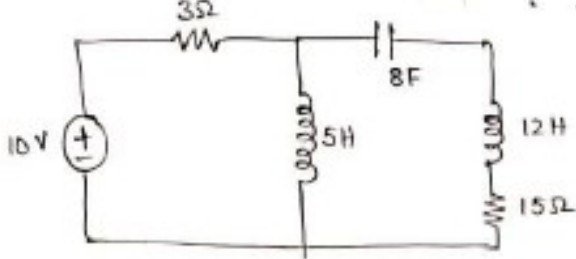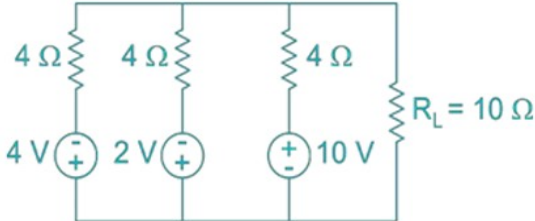Q.No.	Questions	Marks	CO	KL
UNIT-I				
1.	a) Obtain the dual network for the following circuit. 	[7M]	1	
	b) For the incidence matrix shown below, draw the graph. $a \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ 1 & 0 & 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \end{bmatrix}$	[7M]	1	
OR				
2.	a) What is meant by network matrices and also explain the types of network matrices	[7M]	1	
	b) Find the value of current through RL using Millman's theorem 	[7M]	1	
UNIT-II				
3.	a) Two wattmeters connected to a 3-phase motor indicate the total power input to be 12kW. The power factor is 0.6. Determine the readings of each	[6M]	2	
	b) Three impedances of 100 +j80 ohms each are connected in star across a balanced 400 V, 3-phase, 3-wire supply. Find the line currents taken by the load and the voltage across each impedance. Draw a phasor diagram.	[8M]	2	
OR				
4.	a) Derive the relationship between phase and line voltages and currents in delta connected three phase system and also draw the phasor diagram.	[10M]	2	



	b)	Write the advantages of 3- $\phi$ circuits over 1- $\phi$ circuits.	[4M]	2	
UNIT-III					
5.	a)	What are the initial conditions? Why are they needed? Explain	[7M]	3	
	b)	Derive the Transient Response of series RLC-circuit with D.C excitation	[7M]	3	
OR					
6.	a)	Explain about the transient response of series RL circuit to the AC excitation for zero initial conditions	[7M]	3	
	b)	Derive the expression for the current in a series RC circuit ( $R = 10\Omega$ , $C = 5\mu\text{F}$ ) excited by a sinusoidal voltage of 230V, 50 Hz if the supply is connected at $t = 0$ . Assume zero initial conditions.	[7M]	3	
UNIT-IV					
7.	a)	Show that the resonant frequency circuit $f_r^2 = f_1 f_2$ where $f_1$ and $f_2$ are the half power frequencies and $f_r$ is the resonant frequency	[7M]	4	
	b)	Explain about Series resonance with phasor diagrams	[7M]	4	
OR					
8.	a)	Obtain the expression for resonant frequency, bandwidth and Q-factor for parallel R-L-C circuit.	[7M]	4	
	b)	Explain about Parallel resonance with phasor diagrams.	[7M]	4	
UNIT-V					
9.	a)	Express h parameters in terms of ABCD parameters	[7M]	5	
	b)	Find the Z- parameters for the following circuit.	[7M]	5	
OR					
10.	a)	Express Z parameters in terms of ABCD parameters	[7M]	5	
	b)	Find the ABCD and h - parameters for the following circuit	[7M]	5	

\*\*\*\*\*