

HALL TICKET NUMBER

--	--	--	--	--	--	--	--	--	--

PACE INSTITUTE OF TECHNOLOGY & SCIENCES::ONGOLE
(AUTONOMOUS)

II B.TECH I SEMESTER END SUPPLEMENTARY EXAMINATIONS, MARCH/APRIL - 2023
ELECTRICAL CIRCUIT ANALYSIS
(EEE Branch)

Time: 3 hours

Max. Marks: 60

Note: Question Paper consists of Two parts (Part-A and Part-B)



PART-A




Answer all the questions in Part-A (5X2=10M)

Q.No.	Questions	Marks	CO	KL
1	a) State the maximum power transfer theorem for AC circuits.	[2M]	1	1
	b) Explain the advantages of poly phase system over single phase system	[2M]	2	1
	c) What is the significance of Dot Convention?	[2M]	3	1
	d) Describe the equations of Admittance parameters	[2M]	4	1
	e) What is the principle of duality of an electrical network	[2M]	5	1

PART-B

Answer One Question from each UNIT (5X10=50M)

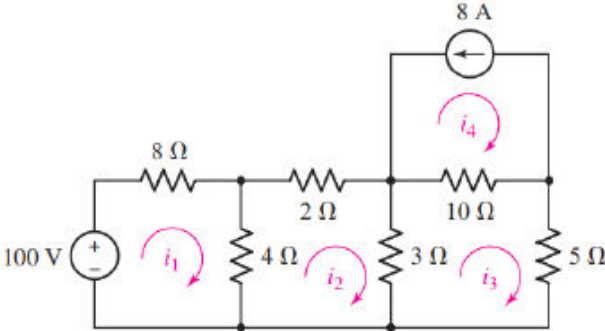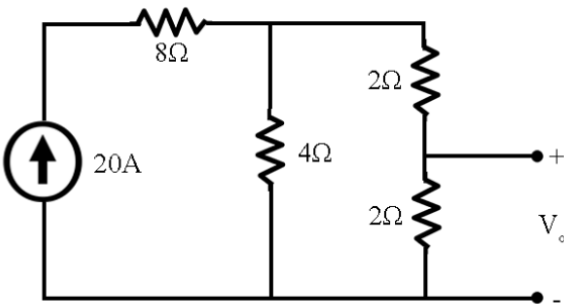Q.No.	Questions	Marks	CO	KL
UNIT-I				
2.	By using the mesh analysis determine the loop currents in the following circuit shown in Figure – 1	[10M]	1	4
				
Figure – 1				
OR				
3.	a) State and explain Norton's Theorem.	[5M]	1	1
	b) Verify the reciprocity theorem for the circuit shown in figure – 2	[5M]	1	1
				
Figure – 2				

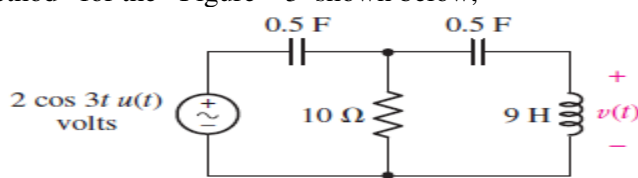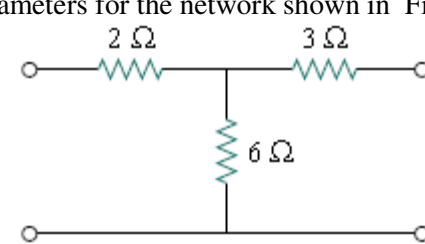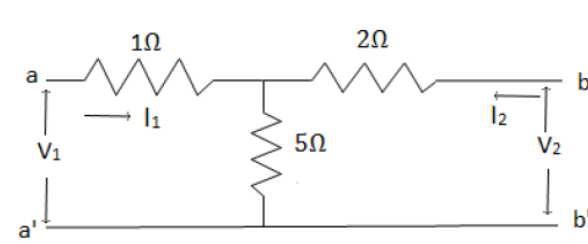UNIT-II					
4.	a)	Show that $V_L = V_{ph}$, $I_L = 1.732 I_{ph}$ for a 3 phase delta connected balanced load. .	[5M]	2	2
	b)	Each phase of a balanced star-connected load consists of $R = 10 \text{ ohm}$ and $C = 10 \mu\text{F}$. Calculate the line currents and total real and reactive powers when a symmetrical 415 V , 50 Hz, three-phase supply is applied to it.	[5M]	2	2
OR					
5.	a)	Show that 2 wattmeter are sufficient to measure 3 phase total power even when the load was unbalanced	[5M]	2	2
	b)	A balanced delta-connected three-phase load absorbs a complex power of 100 kVA with a lagging power factor of 0.8 when the r.m.s line to line voltage is 2400 V. Calculate the impedance of each arm of the delta-connected load.	[5M]	2	3
UNIT-III					
6.	a)	Two coils with inductances in the ratio of 5 : 1 have a coupling coefficient $k = 0.5$. When these coils are connected in Series aiding, the equivalent inductance is 44.4 mH. Find L_1 , L_2 and M .	[6M]	3	3
	b)	Analyze the transient response for the series RLC circuit with DC excitation	[4M]	3	2
OR					
7.	a)	determine an expression for the voltage $v(t)$ Using Lapalace Transform Method for the Figure – 3 shown below, 	[6M]	3	3
	b)	Derive an expression for the energy stored in a capacitor.	[4M]	3	3
UNIT-IV					
8.	a)	Describe the concept of Z –Parameters	[5M]	4	1
	b)	Find Admittance parameters for the network shown in Figure – 4 	[5M]	4	3
OR					
9.	a)	Find the transmission or general circuit parameters for the circuit shown below. 	[5M]	4	3

	b)	Represent hybrid parameters in terms of transmission parameters and open circuit parameters.	[5M]	4	3
UNIT-V					
10.		For the Resistive Network shown in Figure – 6 , write a cutset schedule and equilibrium equations on voltage basis, hence obtain branch voltages and branch Currents.	[5M]	5	4
<p style="text-align: center;">Figure – 6</p>					
OR					
11.	a)	What is a Cut-Set? List the procedure involved in forming it with a suitable example.	[5M]	5	4
	b)	Draw the graph of a network whose reduced incidence matrix is as shown.	[5M]	5	4
$A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix}$					
