

HALL TICKET NUMBER

--	--	--	--	--	--	--	--	--	--

PACE INSTITUTE OF TECHNOLOGY & SCIENCES::ONGOLE
(AUTONOMOUS)

II B.TECH I SEMESTER END SUPPLEMENTARY EXAMINATIONS, JAN - 2023
NETWORK THEORY
(ECE Branch)

Time: 3 hours

Max. Marks: 60

Note: Question Paper consists of Two parts (Part-A and Part-B)

PART-A




Answer all the questions in Part-A (5X2=10M)

Q.No.	Questions	Marks	CO	KL
1	a) Draw the dual network of RLC series network.	[2M]	1	1
	b) What is co-efficient of coupling? Two inductively coupled coils have self inductances $L_1 = 50$ mH and $L_2 = 200$ mH. If the co-efficient of coupling is 0.8, find the value of the maximum possible mutual inductance.	[2M]	2	1
	c) State maximum power transfer theorem	[2M]	3	2
	d) Derive h-parameters interms of y-parameters	[2M]	4	3
	e) Discuss linearity and superposition principle of laplace transforms	[2M]	5	3

PART-B

Answer One Question from each UNIT (5X10=50M)

Q.No.	Questions	Marks	CO	KL
UNIT-I				
2.	<p>Figure shown an oriented connected graph having 4 nodes and 6 branches. Determine the incidence matrix A.</p>	[10M]	2	2
OR				
3.	a) Write the procedure for tie-set schedule matrix?	[5M]	1	1
	b) Prove the duality condition with an example.	[5M]	4	4
UNIT-II				
4.	a) Explain the concept of self-inductance with a neat diagram	[5M]	2	2

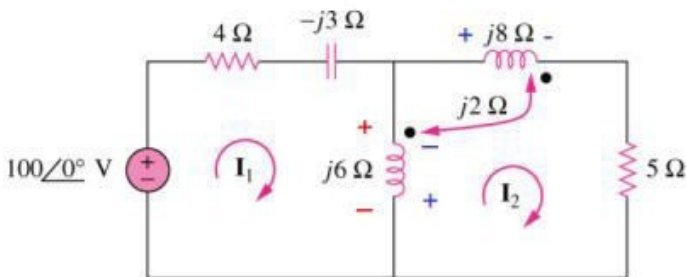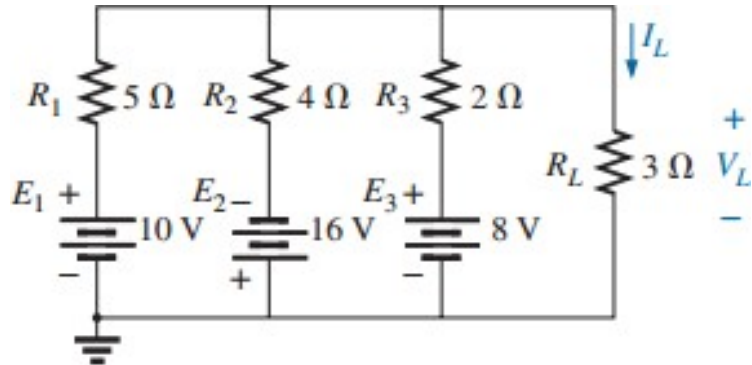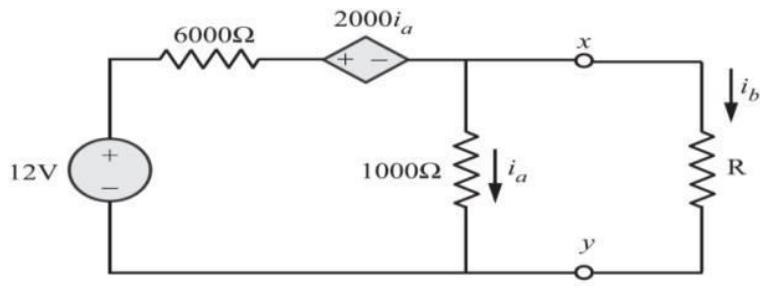	<p>b) Calculate the phasor currents I_1 and I_2 in the circuit of Fig.</p> 	[5M]	2	3
OR				
5.	<p>A series RLC circuit has $R=10\Omega$, $L=0.5H$ and $C=40\mu F$. The applied voltage is 100V. Find.</p> <p>a) Resonant frequency b) Quality factor of coil c) Band width d) Upper and lower power frequencies e) Current at half power frequencies</p>	[10M]	3	3
UNIT-III				
6.	<p>a) Find the current I_L. Use millmans theorem.</p> 	[5M]	3	2
	<p>b) Explain maximum power transfer theorem with an example</p>	[5M]	3	2
OR				
7.	<p>In the circuit shown in <i>Figure</i>. Find the value of i_b using <i>Norton</i> equivalent circuit. Take $R=667\Omega$</p> 	[10M]	3	2
UNIT-IV				
8.	<p>a) Derive the relationship between Z and Y parameters.</p>	[5M]	4	3

	b)	Find the hybrid parameters of the circuit given in Figure .	[5M]	4	3
OR					
9.	a)	Find the z-parameters of the two port network shown in figure below.	[5M]	4	2
	b)	Explain transmission line parameters for two-port networks.	[5M]	4	2
UNIT-V					
10.		In the circuit in Fig. , determine the current $i(t)$ when the switch is changed from position 1 to position 2 at $t = 0$ section.	[10M]	5	3
OR					
11.	a)	Derive the current expression in a R – C series circuit by DC excitation.	[5M]	5	3
	b)	Derive the current expression in a R – L series circuit by DC excitation.	[5M]	5	3
