

Code No: P21ECT05

HALL TICKET NUMBER

--	--	--	--	--	--	--	--	--	--



PACE INSTITUTE OF TECHNOLOGY & SCIENCES::ONGOLE
(AUTONOMOUS)

II B.TECH I SEMESTER END SUPPLEMENTARY EXAMINATIONS, MARCH/APRIL - 2023
PULSE AND DIGITAL CIRCUITS
(ECE Branch)

Time: 3 hours

Max. Marks: 70

Answer all the questions from each UNIT (5X14=70M)

Q.No.	Questions	Marks	CO	KL
UNIT-I				
1.	a) Define the rise time? Prove that the rise time of low pass RC circuit is $2.2RC$.	[7M]	1	2
	b) A pulse of amplitude 5V and duration 0.5msec is applied to High-pass RC circuit having $R=22K$ and $C=0.47\mu F$. Sketch the output wave form and determine the percentage tilt in the output.	[7M]	1	3
OR				
2.	a) Obtain an expression for gain of an RC high pass circuit excited by a sine wave input.	[7M]	1	3
	b) An RC differentiator circuit is driven by a 1KHz symmetrical square wave of 10V Peak-to peak. Calculate the output voltage levels under steady state if, $RC = 1msec$	[7M]	1	2
UNIT-II				
3.	a) Analyze a positive series clipper circuit with necessary waveforms and transfer characteristics.	[7M]	2	4
	b) A square wave has to generate by passing a sine wave through a clipper. The square wave has to have an upper level of 40 V and a lower level of -20 V. The period of square wave is 5 ms. Draw necessary clipper circuit and output waveforms.	[7M]	2	3
OR				
4.	a) Analyze the positive clamper circuit.	[7M]	2	4
	b) A 100 V peak square wave with a period of 20 ms, is to be negatively clamped at 25 V. Draw the circuit diagram necessary for this purpose. Draw the output waveform.	[7M]	2	3
UNIT-III				
5.	a) Discuss transistor switching times.	[7M]	3	2
	b) How to overcome loading effect in fixed bias binary.	[7M]	4	2
OR				
6.	a) Show that a monostable multivibrator can be used as a voltage to time converter.	[7M]	4	2
	b) Describe the working of two diode sampling gates.	[7M]	4	2
UNIT-IV				
7.	Derive an expression for slope error, displacement error, transmission error and obtain a relation between them for exponential sweep circuit.	[14M]	4	3
OR				
8.	a) What are the different methods of generating time-base waveforms? Explain about each briefly.	[7M]	4	2



	b)	Explain the working of Transistor Miller sweep circuit. What are its advantages over Bootstrap sweep circuits?	[7M]	4	2
UNIT-V					
9.	a)	Realize a three-input NAND gate using transistor transistor logic and explain its operation with the help of truth table.	[7M]	5	3
	b)	Design and explain 2-input ECL OR/NOR gate.	[7M]	5	3
OR					
10.	a)	Discuss the characteristics of logic family.	[7M]	5	3
	b)	Realize a two-input NAND gate using diode transistor logic and explain its operation with the help of truth table.	[7M]	5	2
